

Elevator Control System

8086 Inputs

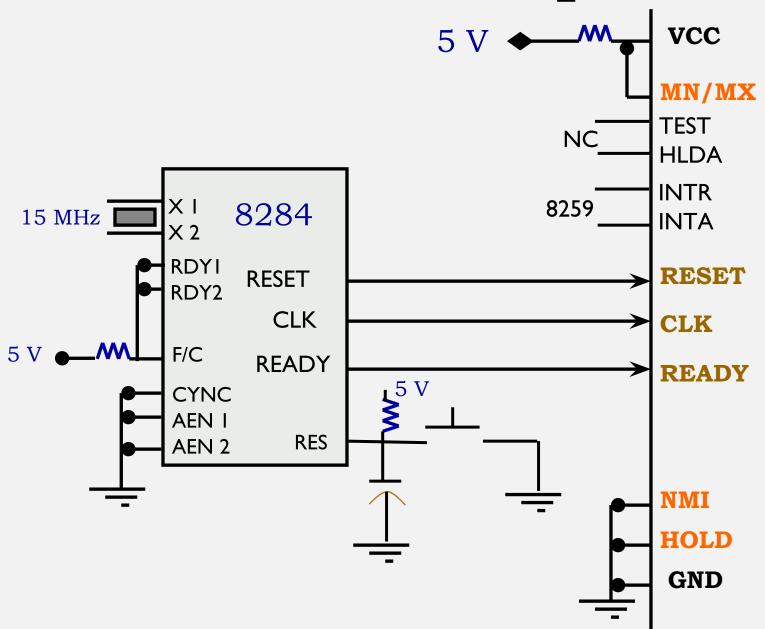

System Bus of 8086 (Address)

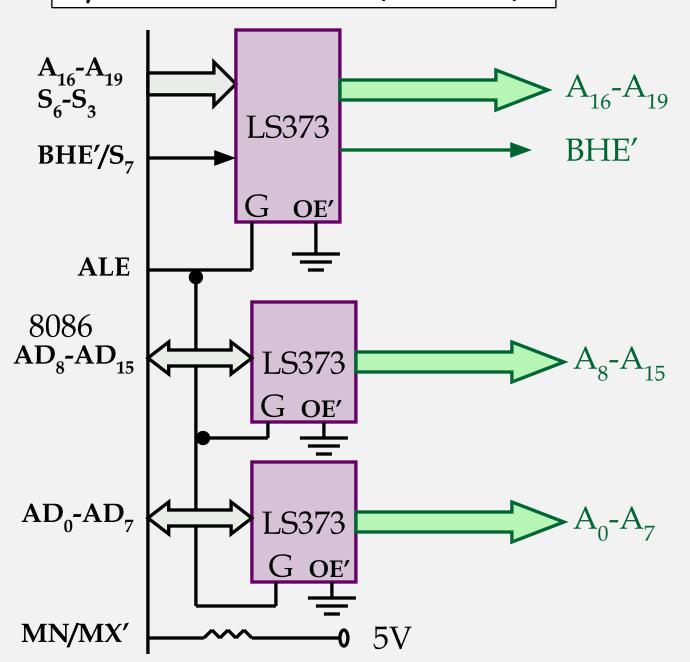


System Bus of 8086(Data + Control) ► MEMR \overline{RD} ► **MEMW LOGIC** LS244 \overline{WR} **CIRCUIT** ► IOR IO/M OE' **IOW** 8086 AD₈-AD₁₅ LS245 $D_{8}-D_{15}$ DT/R' DIR OE' **DEN'** AD₀-AD₇ LS245 $D_0 - D_7$ **DIR** OE' MN/MX' 5V







M/IO'	RD'	WR'	Bus cycle
1	0	1	MEMR'
1	1	0	MEMW'
0	0	1	IOR'
0	1	0	IOW'

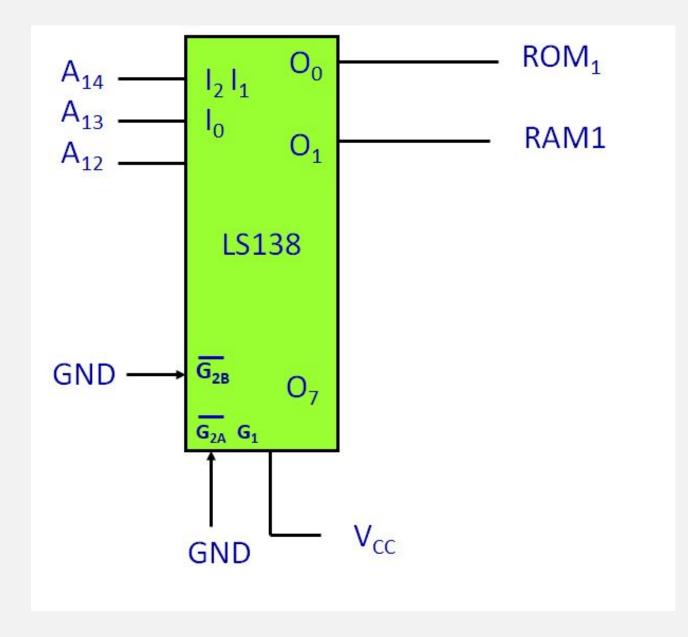



MEMORY INTERFACING

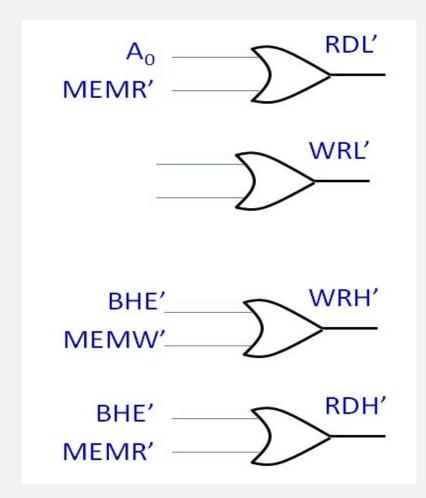


MEMORY INTERFACING

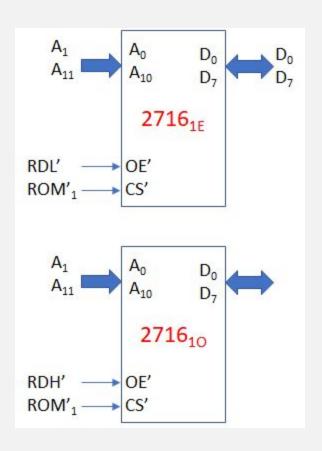

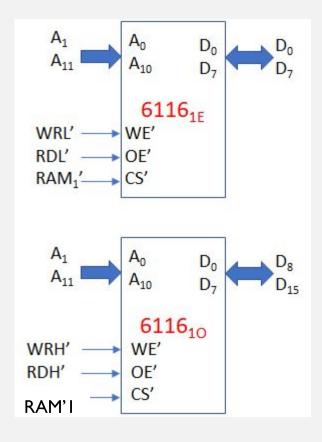


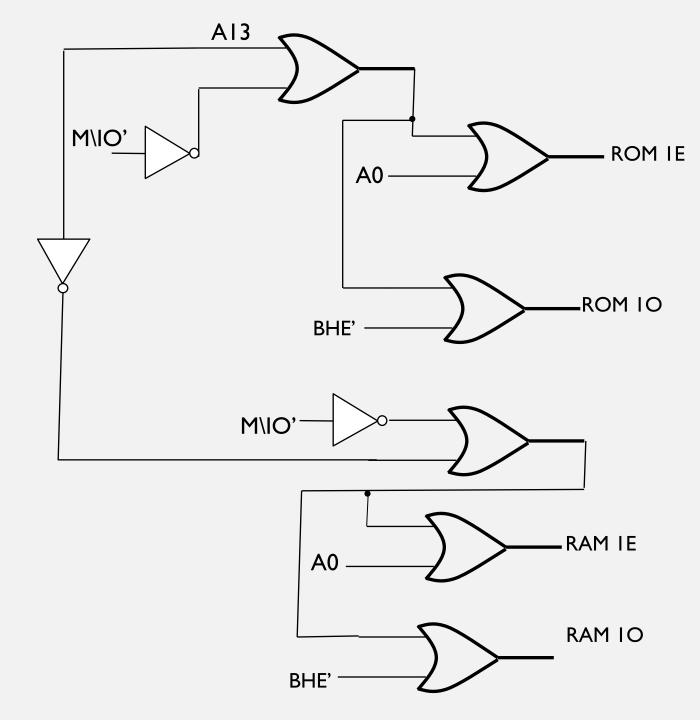


MEMORY INTERFACING

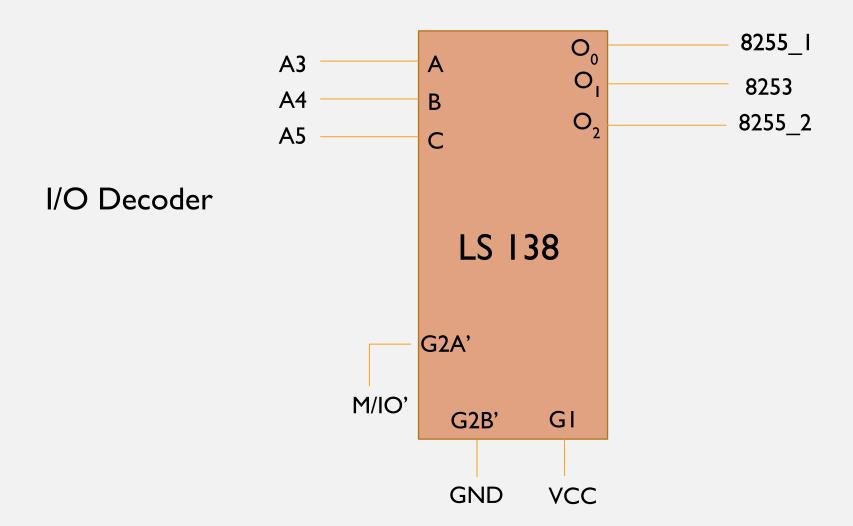


8253 Interfacing

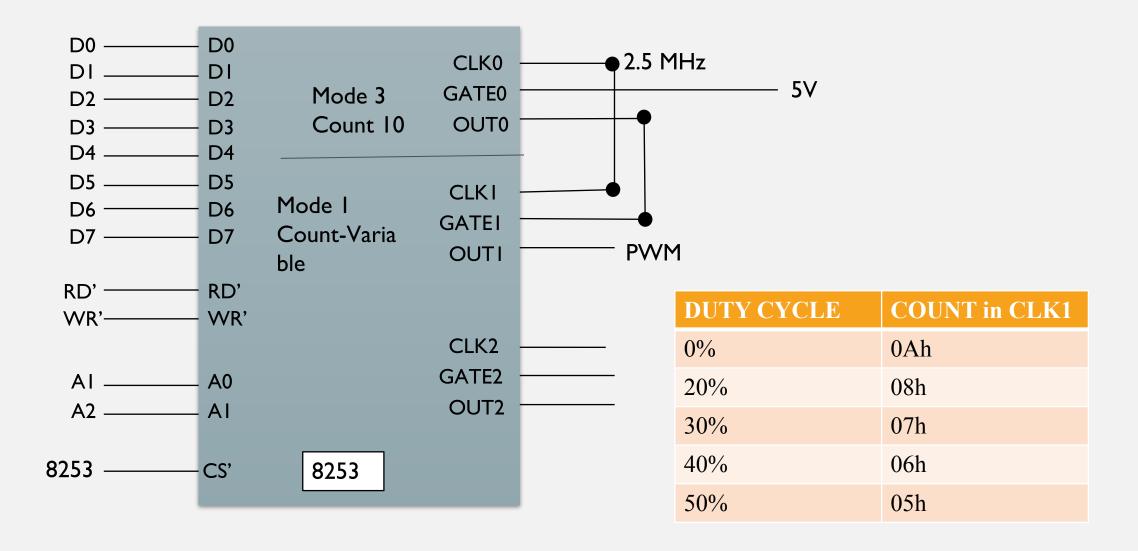

Push Button

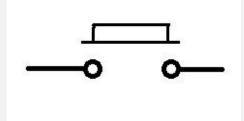


KEYBOARD INTERFACING

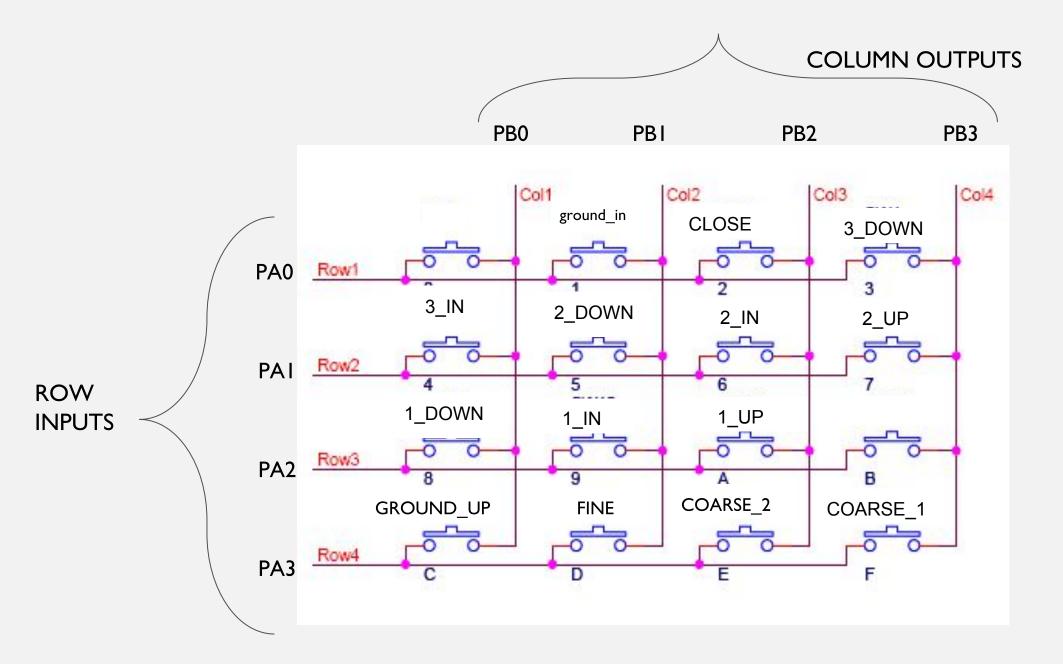



R3	R2	R1	R0	C3	C2	C 1	C0	Hex	Button
0	1	1	1	0	1	1	1	77	Cs_1
0	1	1	1	1	0	1	1	7B	Fine
0	1	1	1	1	1	0	1	7D	Cs_2
0	1	1	1	1	1	1	0	7 E	Ground_up
1	0	1	1	1	0	1	1	BB	First_up
1	0	1	1	1	1	0	1	BD	First_in
1	0	1	1	1	1	1	0	BE	First_down
1	1	0	1	0	1	1	1	D7	2_UP
1	1	0	1	1	0	1	1	DB	2_IN
1	1	0	1	1	1	0	1	DD	2_DOWN
1	1	0	1	1	1	1	0	DE	3_IN
1	1	1	0	0	1	1	1	E7	3_DOWN
1	1	1	0	1	0	1	1	EB	CLOSE
1	1	1	0	1	1	0	1	ED	Ground_in


7 Segment Display

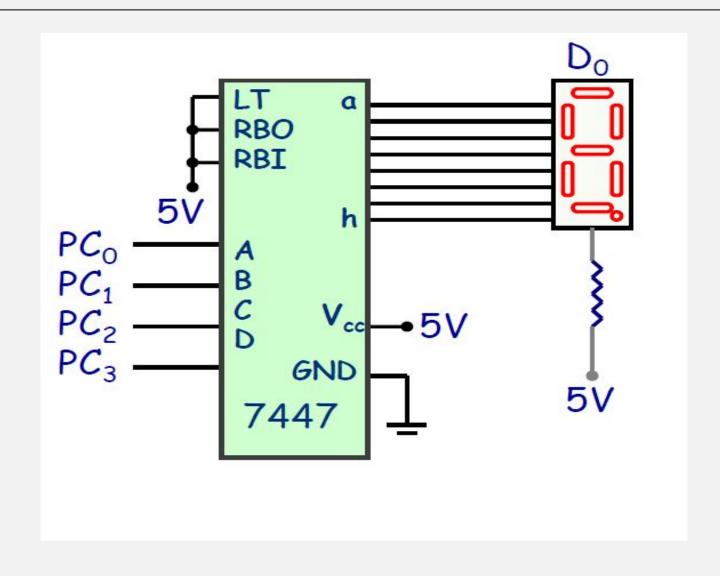

MOTOR INTERFACING

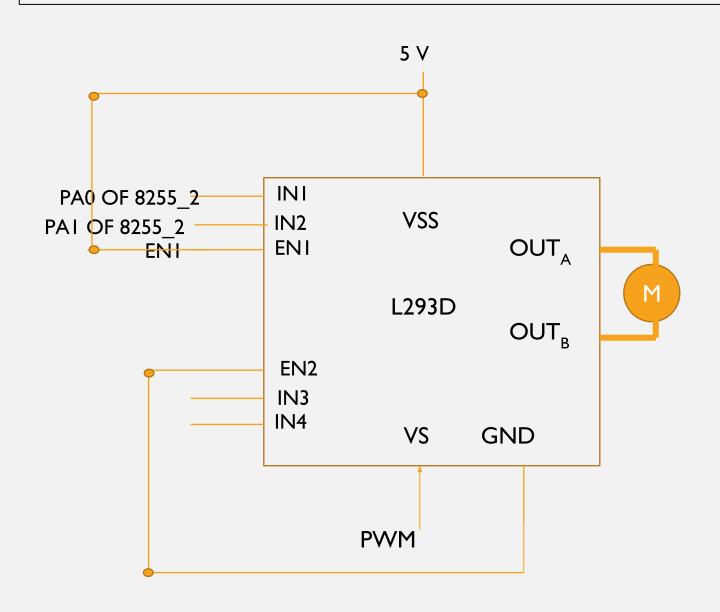

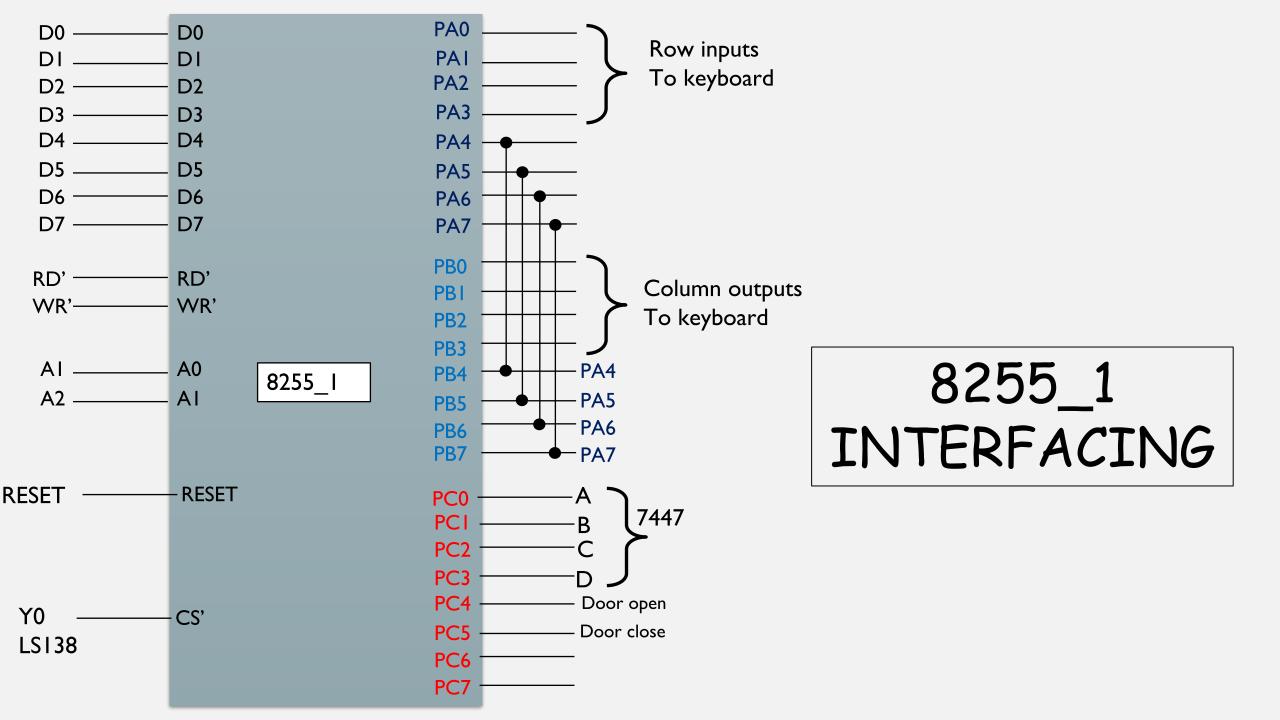

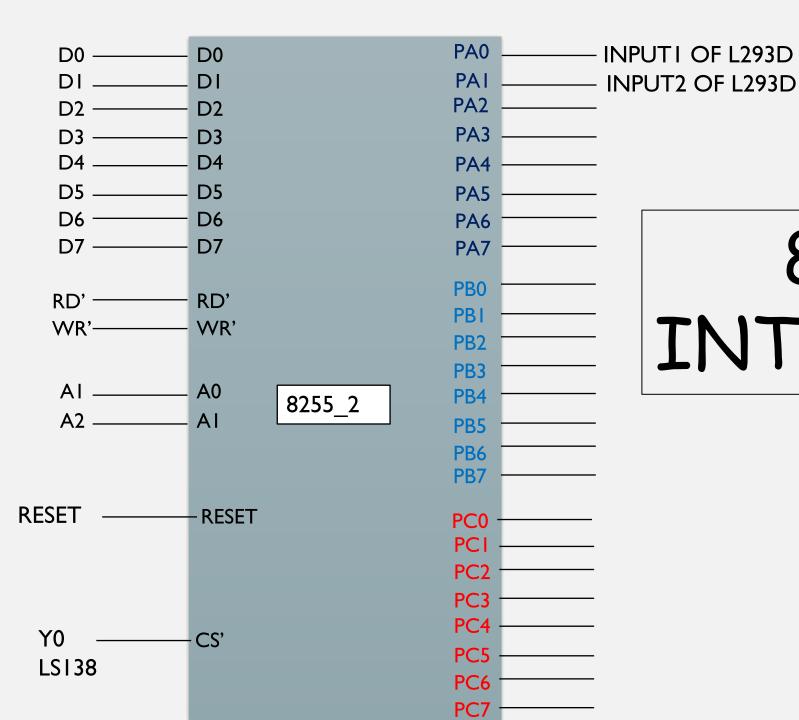

8255_2 INTERFACING